

Day 3

Combinational - Assignment.

i) Implement the following functions using i) 2:1 MUX and NOT gates (ii) 4:1 MUX.

a) $F(A, B, C) = \bar{A}C + B\bar{C}$

$\Rightarrow$ i)

$$= \bar{A}C(B + \bar{B}) + (A + \bar{A})B\bar{C}$$

$$= \bar{A}BC + \bar{A}\bar{B}C + AB\bar{C} + \bar{A}B\bar{C}$$


$$= m(1, 2, 3, 6)$$

Truth Table (using 2:1 MUX and NOT gates):


A	B	C	Y(output)
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

$\Rightarrow$

A	B	Y
0	0	C
0	1	1
1	0	0
1	1	$\bar{C}$

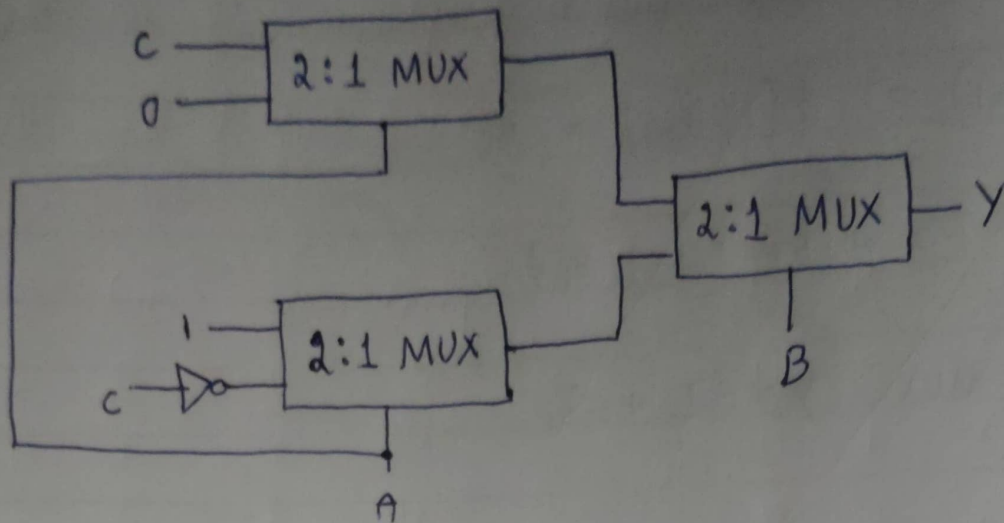

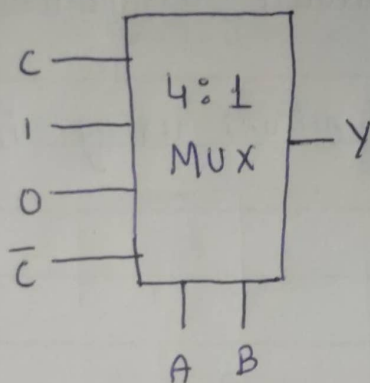ii) Using 4:1 MUX (follow the above truth table)




$$b) F(P, Q, R) = \bar{P}\bar{R} + Q\bar{R} + \bar{P}Q$$

$$\begin{aligned} \Rightarrow i) &= \bar{P}\bar{R}(Q + \bar{Q}) + (P + \bar{P})Q\bar{R} + \bar{P}Q(R + \bar{R}) \\ &= \bar{P}Q\bar{R} + \bar{P}\bar{Q}\bar{R} + P\bar{Q}\bar{R} + \bar{P}Q\bar{R} + \bar{P}Q\bar{R} + \bar{P}Q\bar{R} \\ &= \bar{P}Q\bar{R} + \bar{P}\bar{Q}\bar{R} + P\bar{Q}\bar{R} + \bar{P}Q\bar{R} \end{aligned}$$


$$Y = m(\underline{0}, 2, 3, 6)$$

Truth table (using 2:1 MUX and NOT gate) :

P	Q	R	Y		P	Q	Y
0	0	0	1		0	0	$\bar{R}$
0	0	1	0		0	1	1
0	1	0	1		1	0	0
0	1	1	1	$\Rightarrow$	1	1	$\bar{R}$
1	0	0	0				
1	0	1	0				
1	1	0	1				
1	1	1	0				

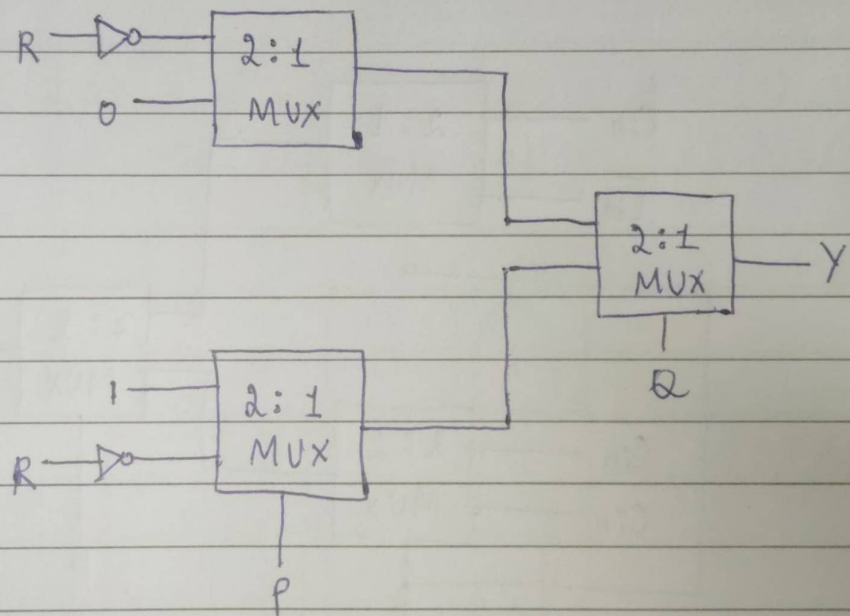

ii) Using 4:1 MUX :

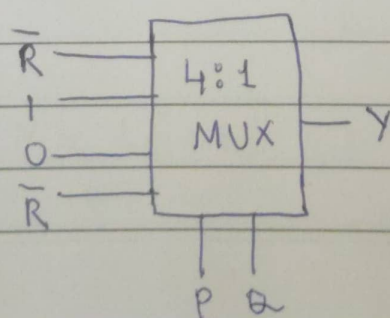


2) Implement the functionality of a full adder using 2:1 Muxes only.


⇒ Truth table of full Adder:

A	B	Cin	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

⇒

A	B	Sum	Carry
0	0	Cin	0
0	1	$\bar{Cin}$	Cin
1	0	$\bar{Cin}$	Cin
1	1	Cin	1

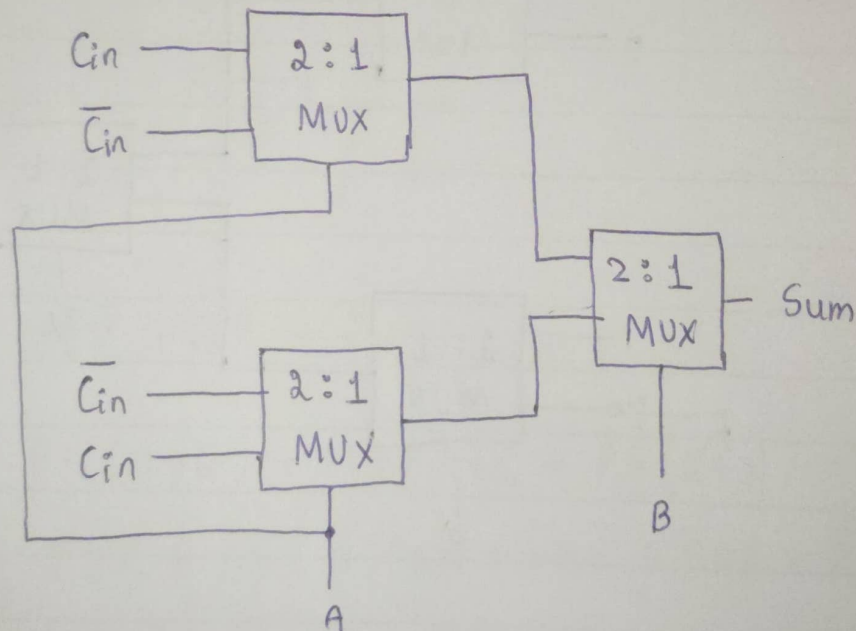

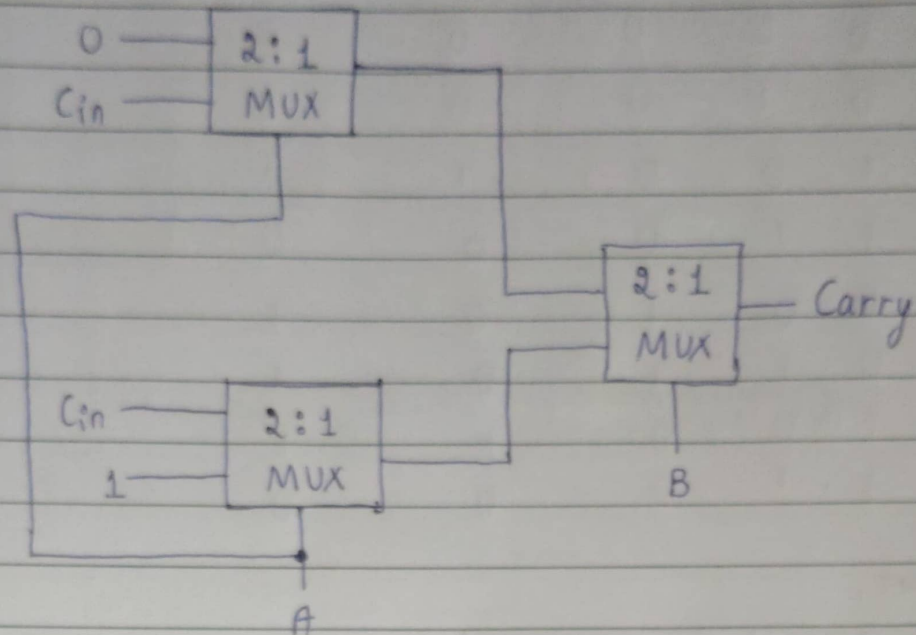

- 3) Simplify $f(a, b, c, d) = \sum m(2, 4, 5, 6, 10) + D(12, 13, 14, 15)$ and implement the SOP expression using 4:1 MUX.

$\Rightarrow$

$ab \backslash cd$	$\bar{c}\bar{d}$	$\bar{c}d$	$c\bar{d}$	cd
$\bar{a}\bar{b}$	0	0	0	1
$\bar{a}b$	1	1	0	1
$a\bar{b}$	X	X	X	X
ab	0	0	0	1

$$Y = \underline{\underline{b\bar{c} + cd}}$$

Let "b" and "c" be select lines,

b	c	d	$b\bar{c}$	$c\bar{d}$	$b\bar{c} + c\bar{d}$
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	1	1
0	1	1	0	0	0
1	0	0	1	0	1
1	0	1	1	0	1
1	1	0	0	1	1
1	1	1	0	0	0

Therefore,

b	c	$b\bar{c} + c\bar{d} = x$
0	0	0
0	1	$\bar{d}$
1	0	1
1	1	$\bar{d}$

